

# ECE 627


## Midterm Examination

May 10, 2013

Open book

In the SAR ADC shown on the next page, initially  $S_1$  and  $S_{z1}$  are closed, as well as  $S_3, S_5, S_7, \dots, S_{19}$ . Then  $S_1$  and  $S_{z1}$  open, and  $S_2$  closes to sample  $V_{in}$  at node A. Afterwards, the switches  $S_3 - S_{20}$  are used to generate the comparison voltages  $V_A$  at node A to find the bits  $b_i$  of the output word. The element values are  $C = 0.4 \text{ pF}$ ,  $C_s = 0.1 \text{ pF}$  and  $R = 1 \text{ k}\Omega$ .  $V_{ref} = 3 \text{ V}$ .

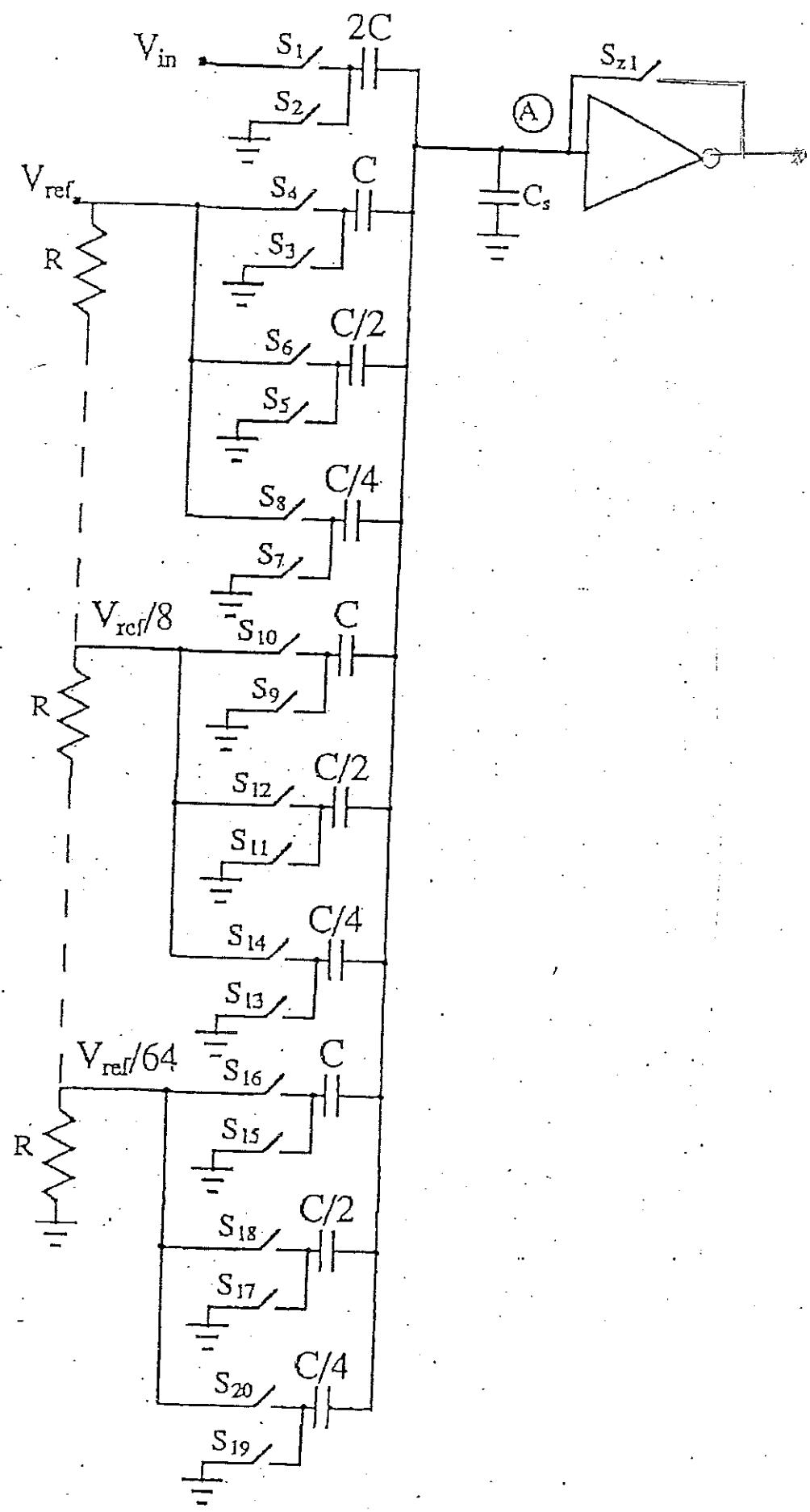
- a. What is the resolution of the ADC?
- b. What are the MSB and LSB voltage steps in  $V_A$ ?
- c. Find the expression for  $V_A$  in terms of  $V_{in}, b_i, C$  and  $V_{ref}$ .
- d. What will be the value of the voltage  $V_A$  after the first 3 MSB cycles if  $V_{in} = 0.8V_{ref}$  ?
- e. What is the worst-case error in  $V_A$  if the resistors have a 1% matching error?
- f. What is the worst-case DNL error if the capacitors have a 0.2% matching error?



## Solutions

(a) By inspection  $N = 9$

(b) MSB step ( $s_3 - s_4$ ):

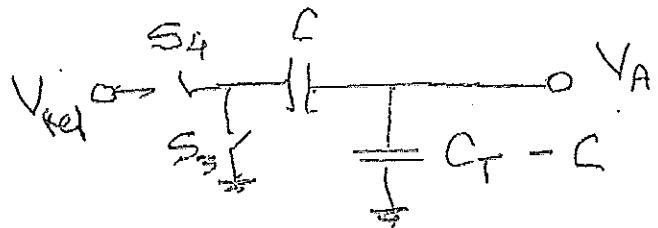

$$\begin{aligned} C_T &= 2C + C_S + 3C(1+0.5+0.25) \\ &= 7.25C + C_S = 3 \text{ pF} \end{aligned}$$

$$\Delta V_{A_{MSB}} = \frac{C}{C_T} V_{ref} = 0.4 \text{ V}$$

$$\Delta V_{A_{LSB}} = \frac{C/4}{C_T} \frac{V_{ref}}{64} = 1.5625 \text{ mV}$$

$$\Delta V_{A_{MSB}} / \Delta V_{A_{LSB}} = 256 = 2^8$$

$$\textcircled{c} \quad \hat{V}_A = (V_{ref} C / C_T) \cdot (b_1 + b_2 2^{-1} + \dots + b_9 2^{-8})$$

For  $V_{in} = 0$

$$= 0.4 \sum_{i=1}^9 b_i 2^{-i+1} = 0.8 \sum_{i=1}^9 b_i 2^{-i} \text{ V}$$

$$\therefore V_A = \hat{V}_A - \frac{2C}{C_T} V_{in} \approx 0.8 \sum_{i=1}^9 b_i 2^{-i} - 0.266 V_{in}$$

$$\textcircled{d} \quad V_A = 0.8(0.5 + 0.25) - 0.64 = -40 \text{ mV}$$

(2) Worst case: R's below  $V_{ref}/8$  too small, above too large (or vice versa). Then, the string current is  $i = V_{ref} / (56.56 + 7.92)$

$$i \approx 46.526 \text{ mA}$$

$$V_8 \triangleq V_{ref}/8 = 0.375 \text{ V} \rightarrow 0.3685 \text{ V}$$

$$V_{64} = V_{ref}/64 \approx 0.0469 \text{ V} \rightarrow 0.04606 \text{ V}$$

In the worst case, all caps at  $V_{ref}/8$  and  $V_{ref}/64$  are critical, so the error in  $V_A$  is

$$\Delta V_A = \frac{C}{C_T} (1 + 0.5 + 0.25) (\Delta V_8 + \Delta V_{64}) =$$

$$\Delta V_A = \frac{0.4}{3} 1.75 (6.5 + 0.24) \text{ mV} \approx 1.413 \text{ mV} > 1.25$$

(3) Worst case: 100...0  $\leftrightarrow$  011...1

assume MSB cap  $C_{MSB} \rightarrow 1.002C$ , and all others  $0.998C_{non}$ . Then  $C_T = 0.998(6.25C + C_S) + 1.002C = 2.9956 \text{ pF}$ . Change in  $V_A$  value:

$$\Delta V_A = V_{ref} \left\{ \frac{1.002C}{C_T} - 0.998(2^1 + \dots + 2^8) \frac{C}{C_T} \right\}$$

$$\Delta V_A = N_{\text{rd}} \frac{C}{C_T} \left[ 1.002 - 0.998 \times (1 - 2^{-3}) \right]$$

$$\approx 0.4006 \times 0.0079 \approx 3.164 \text{ mV} \approx 2 \text{ LSBs}$$