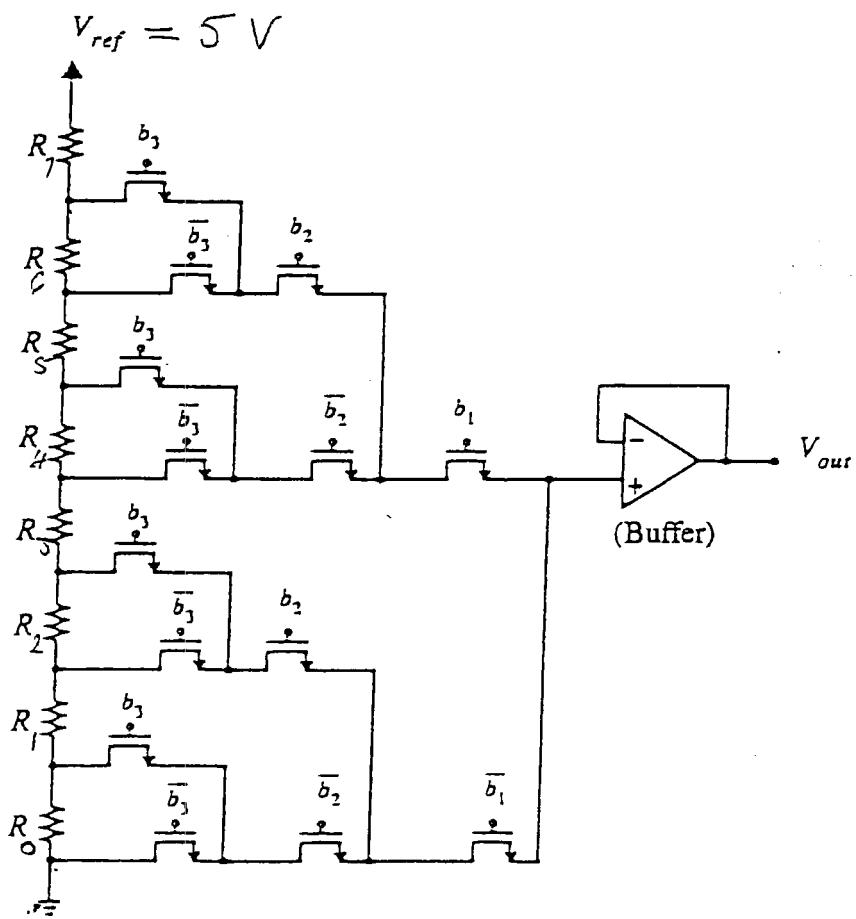


1. In the 3-bit DAC shown, process variations cause the k th resistor to have an error $r_k = 0.02kR_0$ for $k = 1, 2, \dots, 7$.
- What will be the output voltage levels?
 - What will be the DNL, in volts and LSBs?
 - What will be the end-point INL, in volts and LSBs?



$$1. \text{ a. } R_i = R_0 (1 + 0.02 i)$$


$$V_k = V_{\text{ref}} \frac{\sum_{i=0}^{k-1} R_0 (1 + 0.02 i)}{\sum_{i=0}^n R_0 (1 + 0.02 i)} = \frac{V_{\text{ref}} k}{8.56} \left(0.99 + \frac{k}{100} \right)$$

$$\sum_{i=0}^n i = 0 + 1 + \dots + (n-1) + n = \frac{n(n+1)}{2}$$

$$V_0 = 0 \text{ V}, V_1 \approx 0.584 \text{ V}, V_2 \approx 1.18 \text{ V}, \dots$$

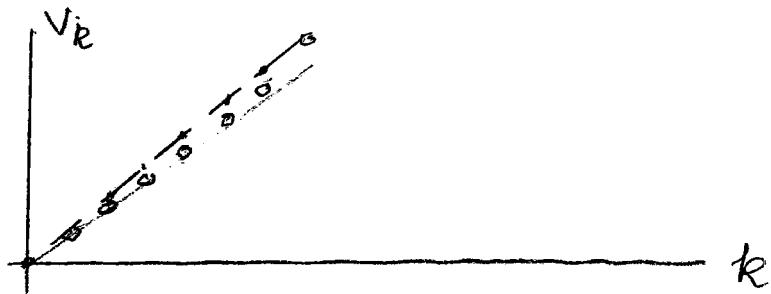b. The largest step occurs between

$$V_6 \neq V_7 : \Delta V_{67} \approx 0.654 \text{ V}.$$



$$V_{LSB} = V_{\text{ref}} 2^{-3} = 0.625 \text{ V}$$

$$\text{DNL}_{\text{max}} = 0.654 - 0.625 = 0.029 \text{ V} \rightarrow 0.046 \text{ LSB}$$

$$\text{c. } \text{INL} = |V_k - k V_7 / 7| =$$


$$= \frac{V_{\text{ref}}}{8.56} k \left[0.99 + \frac{7}{100} - \left(0.99 + \frac{k}{100} \right) \right] =$$

$$= \frac{V_{\text{ref}}}{856} k (7 - k). \quad \frac{d}{dk} \text{INL} \rightarrow 0 \rightarrow k = 3.5$$

$$\text{Max INL for } V_3 \neq V_4 : \frac{5}{856} 12 = 70 \text{ mV} = 0.1125$$

1(60%) For the 4-bit A/D converter shown, $V_{ref} = 2.5$ V and $V_{in} = 1.76$ V. The smallest capacitor in the circuit is 0.5 pF, and the parasitic capacitance C_p is 10 pF. The offset voltage of the op-amp is $V_{os} = 4$ mV.

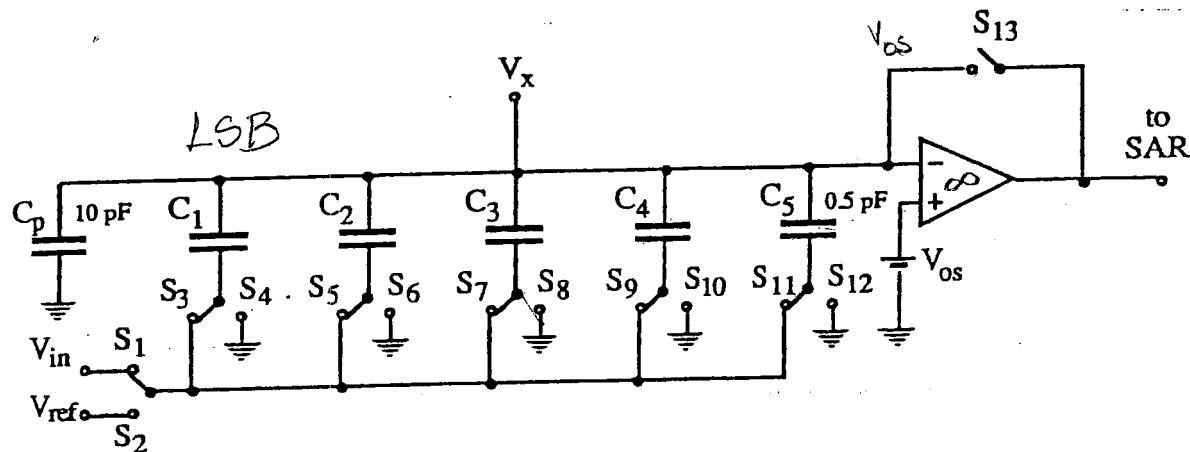- (a) Give all capacitor sizes.
- (b) For each conversion cycle, give the value of V_x and the resulting bit.
- (c) What is the difference between V_{in} and the analog equivalent of the digital output, in volts and in LSB's ?




a) $C_1 = 4.0 \text{ pF}$

$C_2 = 2.0 \text{ pF}$

$C_3 = 1.0 \text{ pF}$

$C_4 = 0.5 \text{ pF}$

b) Let's model the circuit as

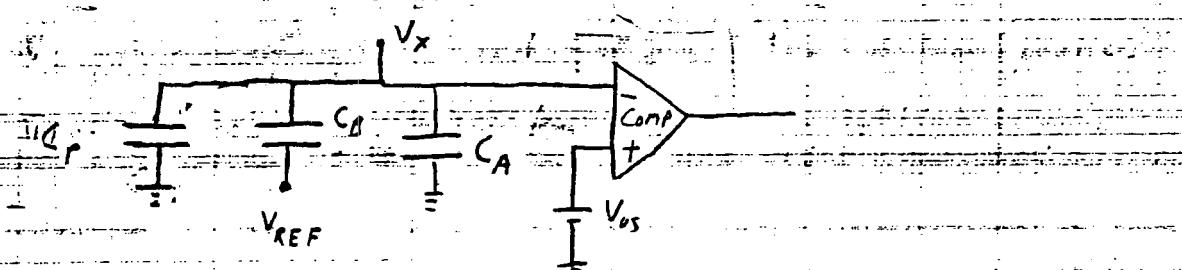

$$q_A = C_A V_x$$

$$q_B = C_B (V_x - V_{REF})$$

$$q_p = C_p V_x$$

$$But \ q_A + q_B + q_p = V_{os} C_p - (V_{in} - V_{os})(C_A + C_B)$$

So

Nice!

$$C_A V_x + C_B (V_x - V_{REF}) + C_p V_x = V_{os} C_p - (V_{in} - V_{os})(C_A + C_B)$$

$$V_x (C_A + C_B + C_p) = V_{REF} C_B + V_{os} C_p + (V_{os} - V_{in})(C_A + C_B)$$

$$V_x = \frac{V_{REF} C_B + V_{os} C_p + (V_{os} - V_{in})(C_A + C_B)}{C_A + C_B + C_p} = 8 + 10$$

Step 1: $C_A = 4 \mu F \quad C_B = 4 \mu F$

(Using Calculator to evaluate)

$$V_x = -0.22 V \quad b_3 = 1 \quad \leftarrow$$

$$-0.22267 V$$

Step 2: $C_A = 2 \mu F \quad C_B = 6 \mu F$

$$V_x = +0.055 V \quad b_2 = 0 \quad \leftarrow$$

Step 3: $C_A = 3 \mu F \quad C_B = 5 \mu F$

$$V_x = -0.084 V \quad b_1 = 1 \quad \leftarrow$$

Step 4: $C_A = 2.5 \mu F \quad C_B = 5.5 \mu F$

$$V_x = -0.014 V \quad b_0 = 1 \quad \leftarrow$$

1011_{binary} 11 decimal

quant. error

$$\left| \left(\frac{11}{16} \cdot V_{REF} \right) - V_{in} \right| = 0.04125 V$$

or $\frac{0.04125 V}{2.5 V} \text{ LSB's} = 0.264 \text{ LSB}$