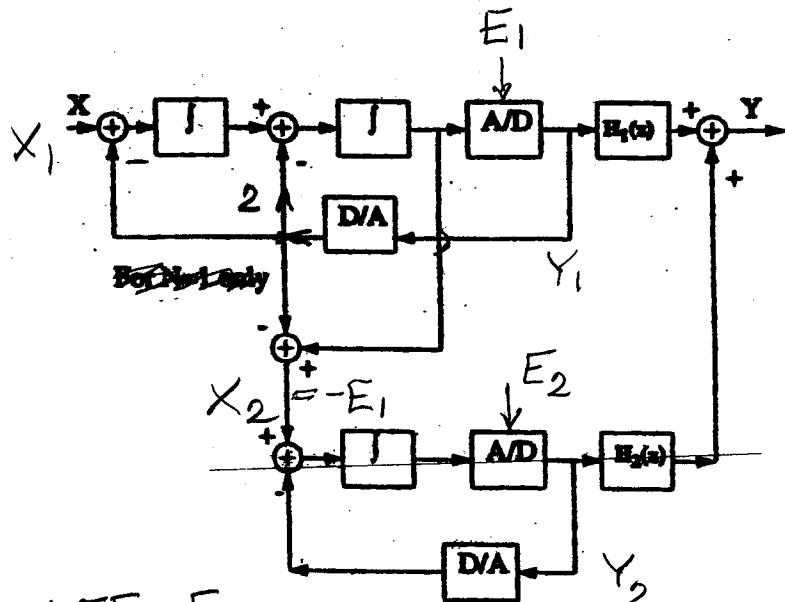


HOMEWORK 5

WHAT SHOULD BE THE TRANSFER FUNCTIONS OF  $H_1$  AND  $H_2$  IN THE 2+1 MASH SHOWN BELOW SO THAT THE INPUT  $X$  APPEARS IN  $Y$  UNDISTORTED, AND THE QUANTIZATION ERROR OF THE FIRST STAGE IS CANCELLED? WHAT ARE THE NTF AND STF FOR THE WHOLE SYSTEM?

ASSUME THAT THE TRANSFER FUNCTION OF THE INTEGRATORS IS  $I(z) = \frac{z^{-1}}{1-z^{-1}}$



$$Y_1 = STF_1 \cdot X_1 + NTF_1 \cdot E_1$$

$$Y_2 = STF_2 \cdot (-E_1) + NTF_2 \cdot E_2$$

$$Y_1 = E_1 + I[-2Y_1 + I(X_1 - Y_1)] = E_1 + I^2X_1 - (2I + I^2)Y_1$$

$$Y_1 = (1+I)^{-2} (E_1 + I^2X_1) = z^{-2}X_1 + (1-z^{-1})^2E_1$$


$$Y_2 = E_2 - I(E_1 + Y_2) \rightarrow Y_2 = -z^{-1}E_1 + (1-z^{-1})E_2$$

$$Y = H_1 [z^{-2}X_1 + (1-z^{-1})^2E_1] + H_2 [-z^{-1}E_1 + (1-z^{-1})E_2]$$

$$H_1(1-z^{-1})^2 - H_2z^{-1} = 0 \rightarrow H_1 = z^{-1}, H_2 = (1-z^{-1})^2$$

$$Y_1 = z^{-3}X_1 + (1-z^{-1})^3E_2$$

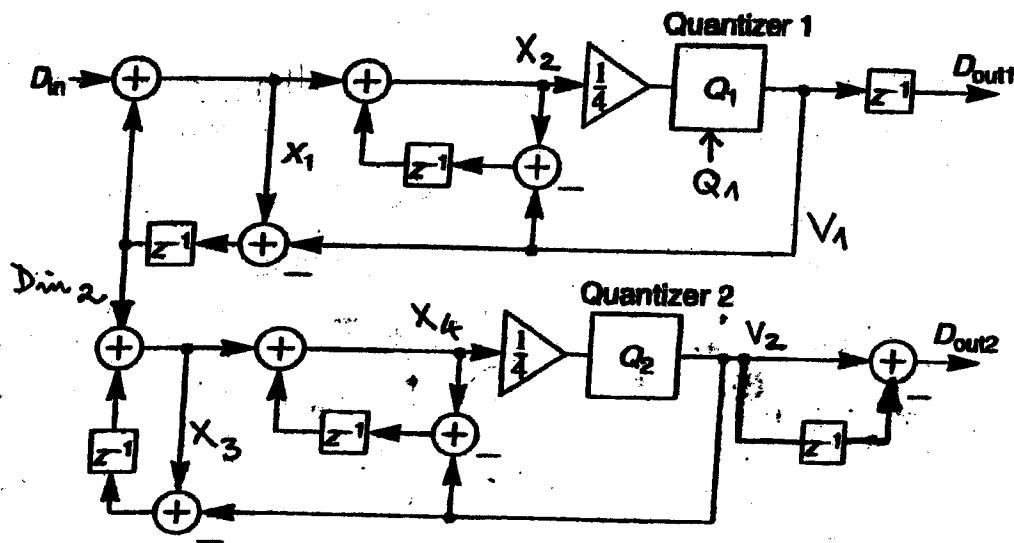CALCULATE THE OUTPUTS  $D_{out1}$  AND  $D_{out2}$  IN TERMS OF THE INPUT  $D_{in}$  AND THE QUANTIZATION ERRORS  $e_1$  AND  $e_2$  FOR THE MASH D/A CONVERTER SHOWN BELOW IN FIG.1.



$$\begin{cases} x_1 = D_{in} + z^{-1}(x_1 - V_1) \Rightarrow x_1 = \frac{D_{in} - z^{-1}V_1}{1 - z^{-1}} \\ x_2 = x_1 + z^{-1}(x_2 - V_1) \Rightarrow x_2 = \frac{x_1 - z^{-1}V_1}{1 - z^{-1}} \\ V_1 = \frac{1}{4}x_2 + Q_1 \end{cases}$$

$$\Rightarrow V_1 = \frac{1}{4} \left\{ \frac{1}{(1-z^{-1})^2} D_{in} + \frac{-z^{-1}-z^{-1}+z^{-2}}{(1-z^{-1})^2} V_1 \right\} + Q_1 = \frac{D_{in}}{4(1-z^{-1})^2} + \frac{z^{-1}(z^{-1}-2)}{4(1-z^{-1})^2} V_1 + Q_1$$

$$\Rightarrow V_1 \underbrace{\left( 4(1-z^{-1})^2 + z^{-1}(2-z^{-1}) \right)}_{4-6z^{-1}+3z^{-2}} = D_{in} + 4(1-z^{-1})^2 Q_1 \Rightarrow V_1 = \frac{D_{in}}{4-6z^{-1}+3z^{-2}} + \frac{4(1-z^{-1})^2}{4-6z^{-1}+3z^{-2}} Q_1$$

$$D_{out1} = z^{-1} \times V_1$$

$$D_{in2} = z^{-1}(x_1 - V_1) = z^{-1} \frac{D_{in} - z^{-1}V_1}{1 - z^{-1}} - z^{-1}V_1 = \frac{z^{-1}}{1 - z^{-1}} (D_{in} - V_1)$$

$$V_2 = \frac{D_{in2}}{4-6z^{-1}+3z^{-2}} + \frac{4(1-z^{-1})^2}{4-6z^{-1}+3z^{-2}} Q_2 =$$

$$= \frac{z^{-1}}{1 - z^{-1}} \times \frac{1}{4-...} D_{in} - \frac{z^{-1}}{1 - z^{-1}} \times \frac{1}{(4-...)^2} D_{in} - \frac{z^{-1}}{1 - z^{-1}} \times \frac{4(1-z^{-1})^2}{(4-...)^2} Q_1 + \frac{4(1-z^{-1})^2}{(4-...)^2} Q_2$$

$$\& D_{out2} = (1-z^{-1}) V_2$$

$$\Rightarrow D_{out2} = \frac{3z^{-1}(1-z^{-1})^2}{(4-6z^{-1}+3z^{-2})^2} D_{in} - \frac{4z^{-1}(1-z^{-1})^2}{(4-6z^{-1}+3z^{-2})^2} Q_1 + \frac{4(1-z^{-1})^3}{4-6z^{-1}+3z^{-2}} Q_2$$

ANALYZE THE CIRCUIT OF FIG.2. WHAT ADDITIONAL TRANSFER FUNCTIONS ARE NEEDED FOR NOISE CANCELLATION BEFORE  $x_3$  AND  $x_6$  CAN BE COMBINED?


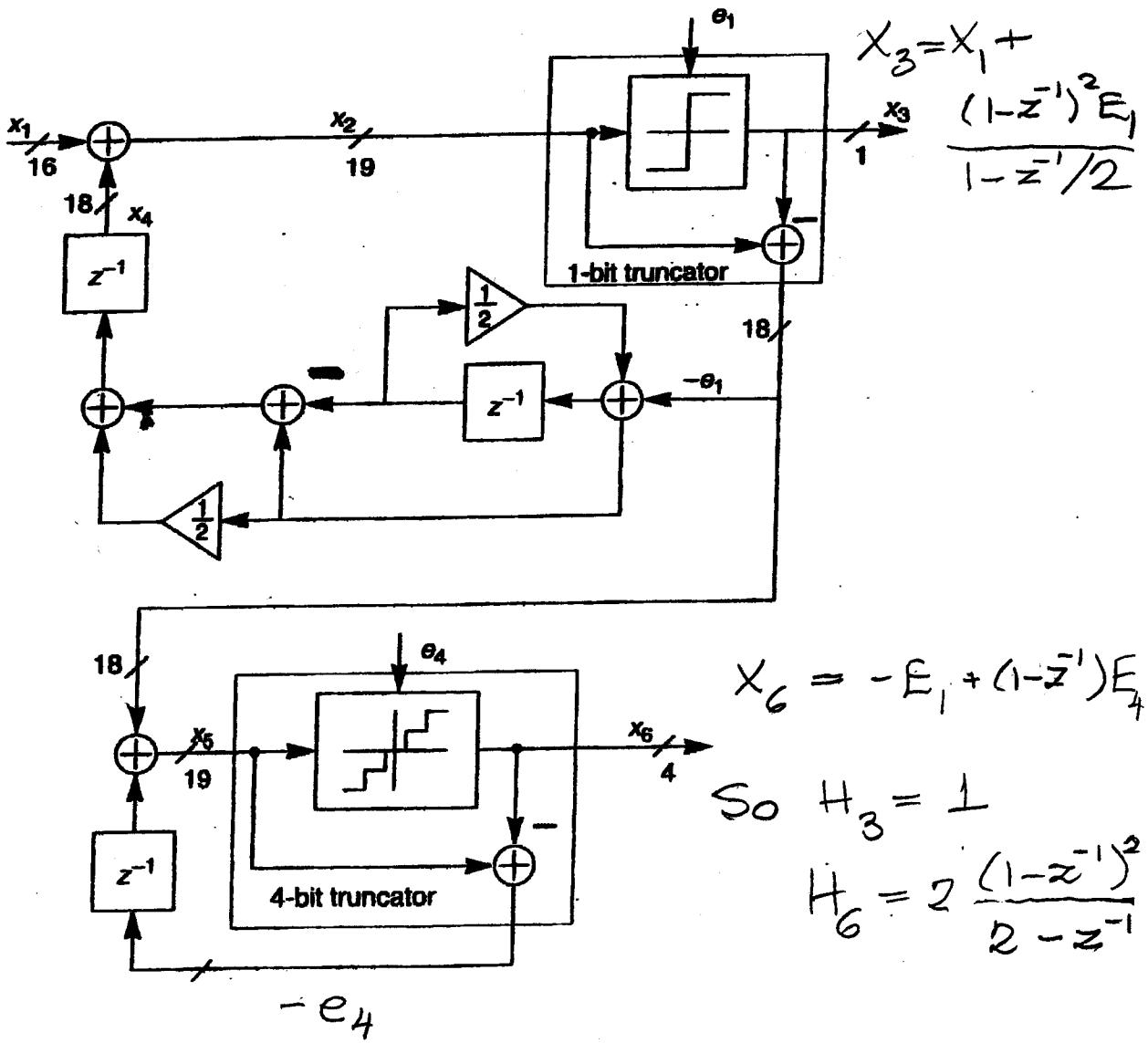


FIG. 2

2(a) For the feedforward delta-sigma loop, find  $b$  such that the signal transfer function is 1.

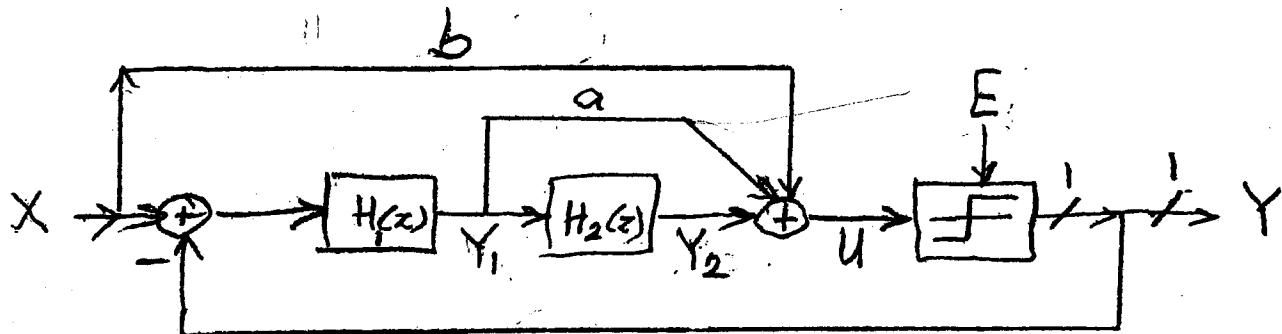2(b) Find  $a$  such that for  $H_1(z) = H_2(z) = \frac{1}{z-1}$ , the noise transfer function is  $(1-z^{-1})^2$ .



$$H_1(z) = H_2(z) = \frac{z^{-1}}{1-z^{-1}}$$

$$Y_1 = H_1(X - Y), \quad Y_2 = H_1 H_2(X - Y)$$

$$\begin{aligned} U &= bX + aY_1 + Y_2 = bX + (a + H_2)H_1(X - Y) \\ &= [b + (a + H_2)H_1]X - (a + H_2)H_1Y = Y - E \end{aligned}$$

$$[1 + (a + H_2)H_1]Y = [b + (a + H_2)H_1]X + E \quad ; \quad b \rightarrow 1 \text{ for undistorted} \quad X$$


$$Y = X + \frac{E}{[ ]} \quad \frac{1}{[ ]} = \frac{1}{1 + aH_1 + H_1^2}$$

Denom. is

$$1 - 2z^{-1} + z^{-2} + az^{-1} - az^{-2} + z^2 \quad \left\{ = \frac{(1-z^{-1})^2}{(1-z^{-1})^2 + az^{-1}(1-z^{-1}) + z^{-2}} \right.$$

For  $a = 2$ , Denom. = 1.

## 2<sup>nd</sup> - order Hairapelian

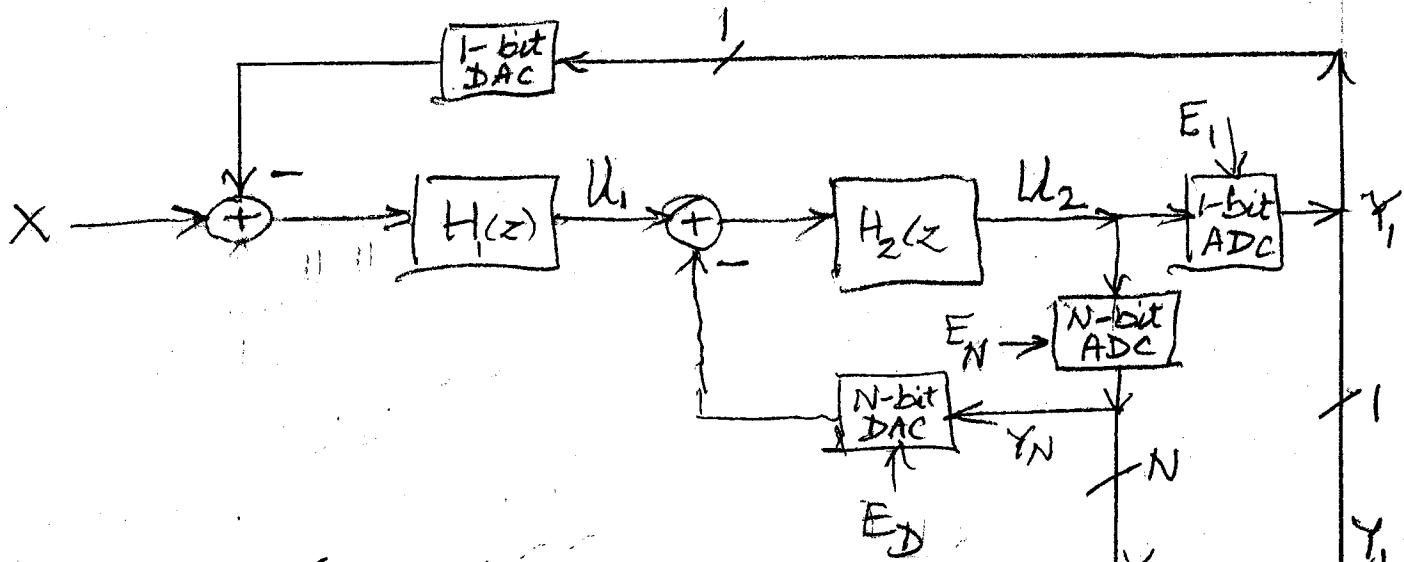

$$U_1 = H_1(X - Y_1)$$

$$U_2 = H_2(U_1 - Y_N - E_D) = H_2 [H_1 X - H_1 Y_1 - Y_N - E_D]$$

$$Y_1 = U_2 + E_1 = H_2 X - H_1 H_2 Y_1 - H_2 Y_N - H_2 E_D + E_1$$

$$Y_N = U_2 + E_N = Y_1 - E_1 + E_N$$

$$Y_1 [1 + H_1 H_2 + H_2] = H_1 H_2 X + (H_2 + 1) E_1 - H_2 E_N - H_2 E_D$$

$$Y_N [ ] = Y_1 [ ] - E_1 [ ] + E_N [ ] =$$

$$Y_N = H_1 H_2 X + E_1 H_1 H_2 + E_N (1 + H_1 H_2) + H_2 E_D$$

To cancel  $E_1$ , multiply  $Y_1$  by  $G_1$  &  $Y_N$  by  $G_N$

$$G_1(H_2 + 1) \stackrel{!}{=} G_N H_1 H_2, \quad G_1 \stackrel{!}{=} F H_1 H_2, \quad G_N = F(H_2 + 1)$$

To transmit  $X$  undistorted, the factor of  $X$  in  $G_1 Y_1 + G_N Y_N$  must be  $z^{-k}$ .

Overall STF

$$(G_L + G_N) \frac{H_1 H_2}{1 + H_1 H_2 + H_2} = F H_1 H_2, \text{ so } F \stackrel{!}{=} z^{-k} / (H_1 H_2)$$

$$G_1 = z^{-k}, \quad G_N = z^{-k} \frac{H_2 + 1}{H_1 H_2}$$