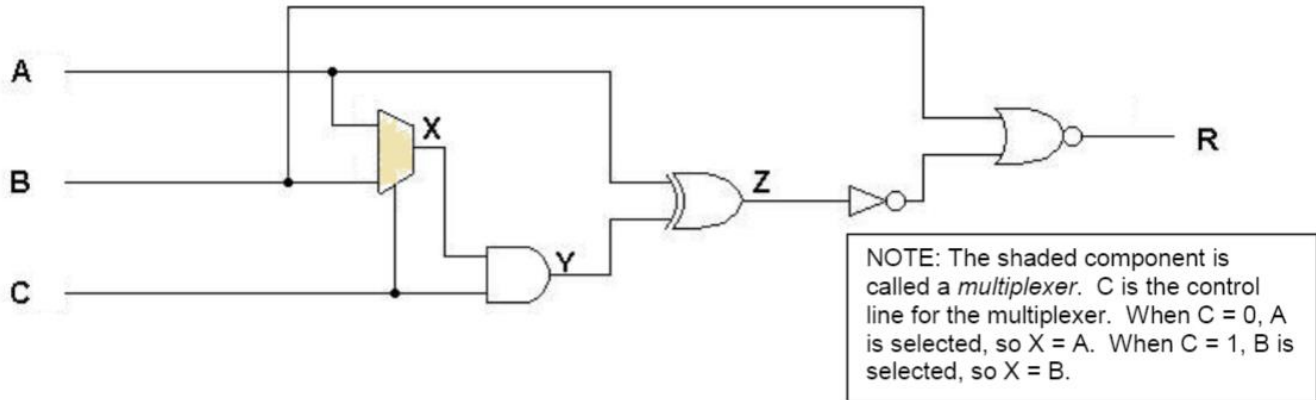


## CS 271 Computer Architecture and Assembly Language

### Self-Check for Lecture#18

Solutions are posted



1. Show the truth table for the circuit shown above. Columns X, Y, and Z are for your convenience if you want to save intermediate results.

A	B	C	X	Y	Z	R
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

2. Find a Boolean equation to describe the circuit shown above.

R =

3. (Optional Challenge) Reduce R to its simplest form. Show your simplification steps.

4. It takes one clock cycle to perform an addition operation in the 4-bit ripple-carry adder (see Lecture slide page 7). How many clock cycles will it take for one addition instruction to be executed in a 64-bit ripple-carry adder?

\_\_\_\_\_ clock cycles

5. The circuit below should be familiar to you, even though it is in a slightly different configuration from the lecture. What does the circuit do? What are the inputs? What results are expected at X and at Y?

