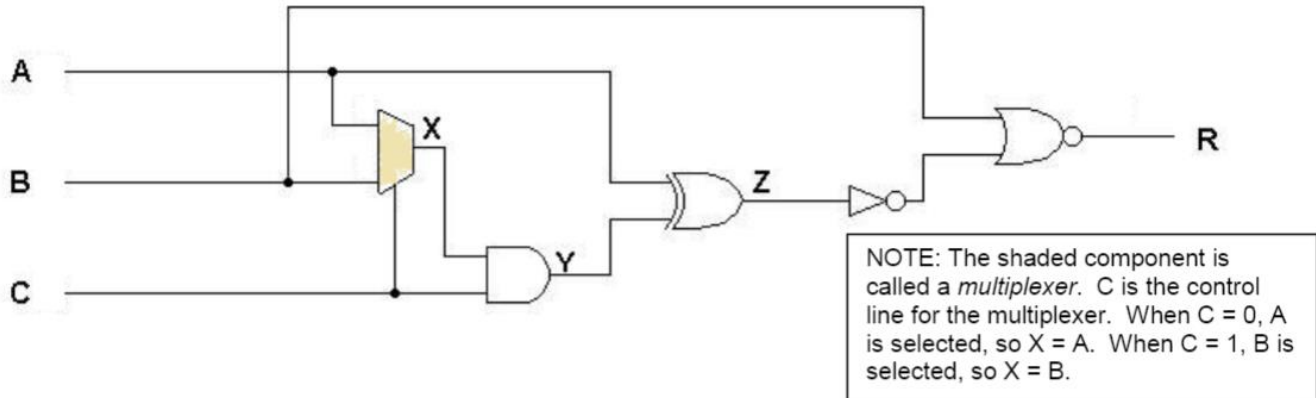


## CS 271 Computer Architecture and Assembly Language

### Self-Check for Lecture#18

Solutions are posted



1. Show the truth table for the circuit shown above. Columns X, Y, and Z are for your convenience if you want to save intermediate results.

A	B	C	x	Y	z	R
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	1	1	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	1
1	1	0	1	0	1	0
1	1	1	1	1	0	0

2. Find a Boolean equation to describe the circuit shown above.

$R = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C}$       Use Lines where R = 1

3. (Optional Challenge) Reduce R to its simplest form. Show your simplification steps.

$R = \overline{A}\overline{B}(\overline{C} + C)$       Distributive Law


$R = \overline{A}\overline{B}(1)$       Inverse Law

$R = \overline{A}\overline{B}$       Identity Law

4. It takes one clock cycle to perform an addition operation in the 4-bit ripple-carry adder (see Lecture slide page 7). How many clock cycles will it take for one addition instruction to be executed in a 64-bit ripple-carry adder?

\_\_\_\_\_ 1 \_\_\_\_\_ clock cycles

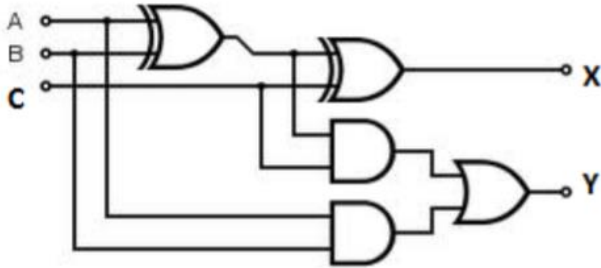5. The circuit below should be familiar to you, even though it is in a slightly different configuration from the lecture. What does the circuit do? What are the inputs? What results are expected at X and at Y?



**It's just a full adder. Inputs A and B are corresponding bits of two binary numbers that are to be added. Input C is "carry in". Output X is the sum bit, and output Y is the "carry out" bit.**