

CS 271

Computer Architecture & Assembly Language

Lecture 18
Digital Logic Circuits
3/3/22, Thursday



Oregon State
University

Odds and Ends

- Due 3/6 11:59 pm
 - Weekly Summary 9

Lecture Topics:

- Digital Logic
- Boolean Logic
- Digital Logic Circuits

Digital Logic

Boolean Logic

What is Digital Logic?

- Discrete circuitry, where the only valid values are a 1 or 0.
- Represented by building blocks of defined functionality.
- An application of boolean logic.

What is Boolean Logic?

- Rules for combining statements that are **TRUE** or **FALSE**
- Examples:
 - If statement A is TRUE, “**not** A” is FALSE
 - If statement A is TRUE, and statement B is TRUE, the combined statement “A **and** B” is also TRUE
 - If statement A is FALSE, and statement B is TRUE, the combined statement “A **or** B” is TRUE

Digital Logic, Boolean Logic, and Truth Tables

- AND, OR, and NOT are logical operators
- Define rules for combining statements that are TRUE and FALSE
- Operators can be defined by truth tables

A	NOT A
F	T
T	F

A	B	A AND B
F	F	F
F	T	F
T	F	F
T	T	T

A	B	A OR B
F	F	F
F	T	T
T	F	T
T	T	T

Boolean Notation

- Boolean variables (e.g., A, B, ...)
 - Can have value of 0 or 1 (false or true)
- Boolean expressions
 - Join Boolean variables with AND, OR, etc.

Functional

NOT(A)

AND(A, B)

OR(A, B)

XOR(A, B)

NAND(A, B)

NOR(A, B)

XNOR(A, B)

Logical

$\sim A$

A AND B

A OR B

A XOR B

A NAND B

A NOR B

A XNOR B

Boolean

A

AB

A+B

$A \oplus B$

\overline{AB}

$\overline{A + B}$

$A \oplus B$

Using Truth Tables

- Define a Boolean function
 - Specify an output for each possible combination of inputs
- Prove that two functions are equivalent
 - Make a truth table for each function
 - Outputs are identical if and only if the functions are equivalent

Truth Tables: 0 = false, 1 = true

2 input, 1 output

$$R = X\bar{Y}$$

X	Y	R
0	0	0
0	1	0
1	0	1
1	1	0

3 input, 1 output

$$R = X+(YZ)$$


X	Y	Z	R
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Internal (electric) Representation of Binary Codes

- Power source
- **Gates** (the “building blocks” with defined functionality)
 - Made of one or more transistors
 - Only 2 voltages are permitted
 - Low (e.g., 0.5v) represents binary 0
 - High (e.g., 5.0v) represents binary 1
 - Can “convert” low \leftrightarrow high using gates
- For any given set of inputs (0s and 1s), gates can be combined to produce specified output (0 or 1).
- These combinations of gates are called **digital circuits**.

- Any desired output can be produced by combinations (circuits) of these 3 gates:

AND

 


Inputs		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

OR



Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

NOT

 

Input	Output
A	C
0	1
1	0

- These additional gates can simplify and/or reduce cost of a circuit



NAND

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0



NOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0



XOR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0



XNOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

Boolean Functions

- A function of n binary variables has 2^n possible combinations of values for the values.
 - E.g., $f(A,B,C)$ has $2^3 = 8$ combinations of values for A, B, and C.
- So ... a function can completely described by its **truth table**.

Example:

- Let $f(A,B,C)$ be defined by the truth table at the right. To write this in Boolean notation
 - Select all rows with $R=1$
 - AND the values in each row, using X for 1, X for 0
 - OR the resulting terms
 - Set $R =$ resulting expression

$$R = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Connection! We have gates that can implement this function as a circuit.
- In its most primitive form:

$$R = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$


Verification

- Test all possible combinations of input to verify that the circuit implements the function

$$R = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1
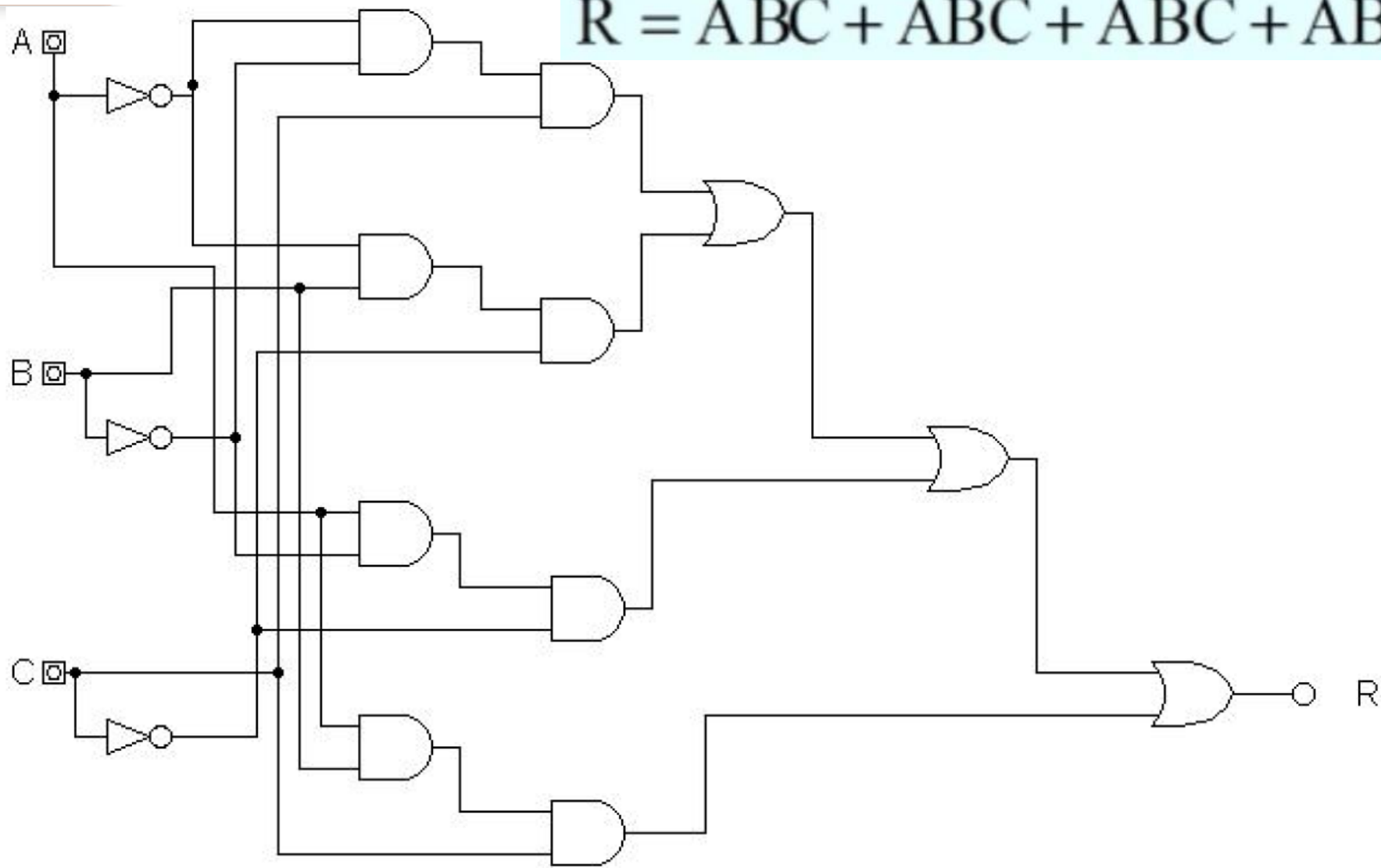
$$R = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$



Simplifications:

- Multiple-input gates
- Equivalent gates
- Use Boolean Logic to simplify the function before implementing the circuit

Boolean Identities

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{\bar{A} + \bar{B}} = \bar{A}\bar{B}$

Definition: $A \oplus B = \bar{A}\bar{B} + \bar{A}B$


Simplify

$$R = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$R = \overline{A}(\overline{B}C + B\overline{C}) + A(\overline{B}\overline{C} + BC) \quad \text{Distributive}$$


$$R = \overline{A}(B \oplus C) + A(\overline{B \oplus C}) \quad \text{Definition, distributive}$$
 
$$R = A \oplus B \oplus C \quad \text{Definition}$$



$$R = A \oplus B \oplus C$$

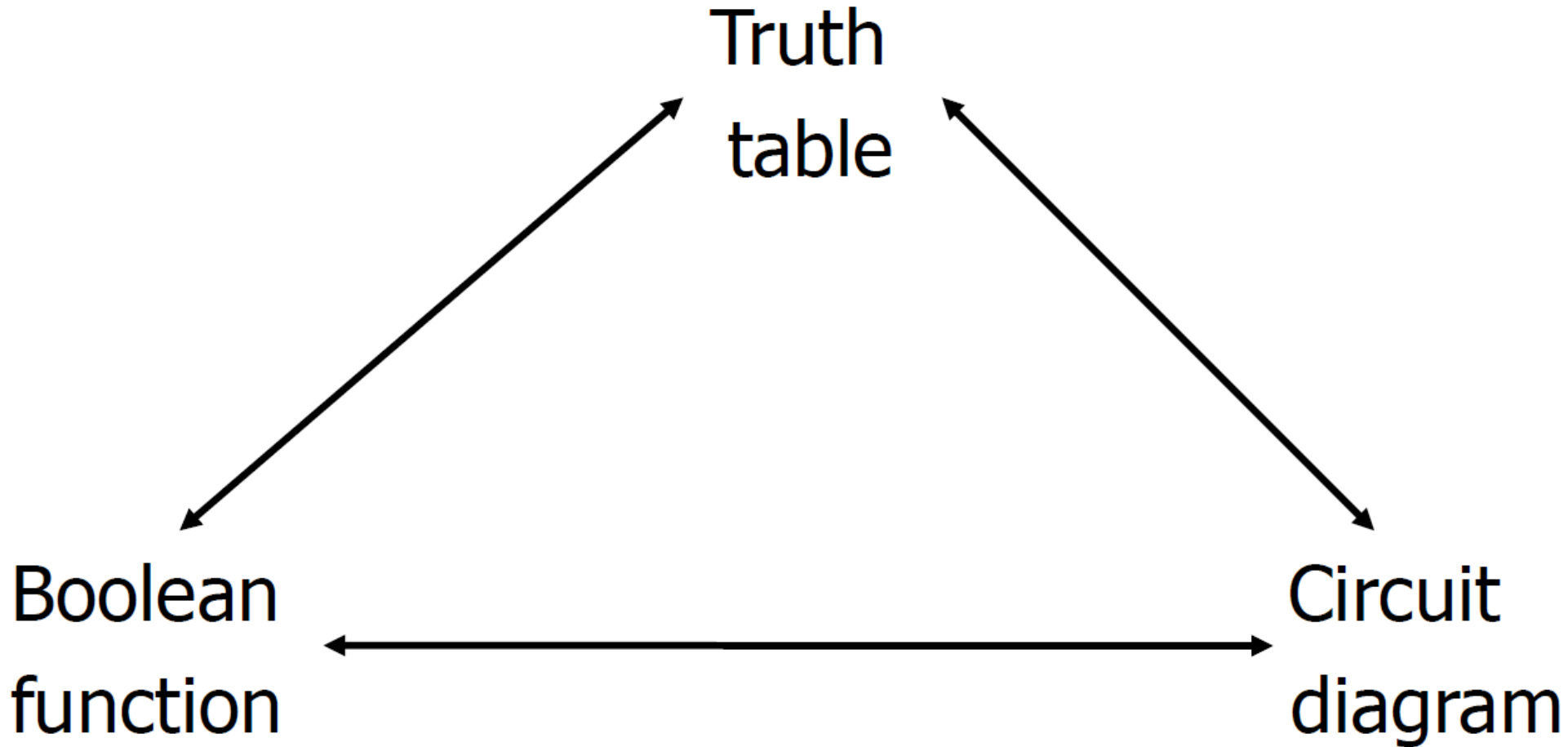Representation of Arithmetic / Logic Circuits




Hardware Circuits


- We are well on our way to showing that an **electrical operation** can be performed on two **electrical numeric representations** to give an **electrical result** that is consistent with the rules of arithmetic.

Digital Logic Circuits

What does this circuit do?

 

4-bit Comparator

 


Adders

- Bitwise addition implements “sum bit” and “carry bit”
- Carry digits “ripple” to next adder
- Half adder: 2 inputs (corresponding bits of two numbers), 2 outputs (sum bit and carry-out bit)
- Full adder: 3 inputs (same as above, plus carry-in bit), 2 outputs (same as above)


Half Adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Full Adder

A	B	Carry in	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

4-bit Ripple Carry Adder

